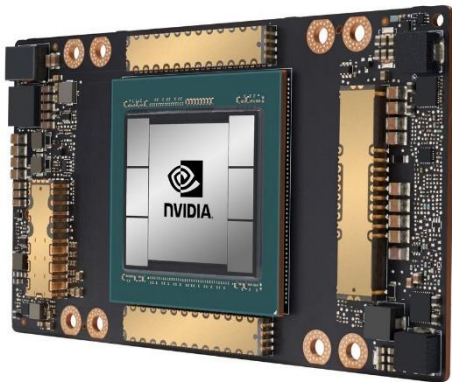



CSCB58: Computer Organization



Prof. Gennady Pekhimenko

University of Toronto

Fall 2020

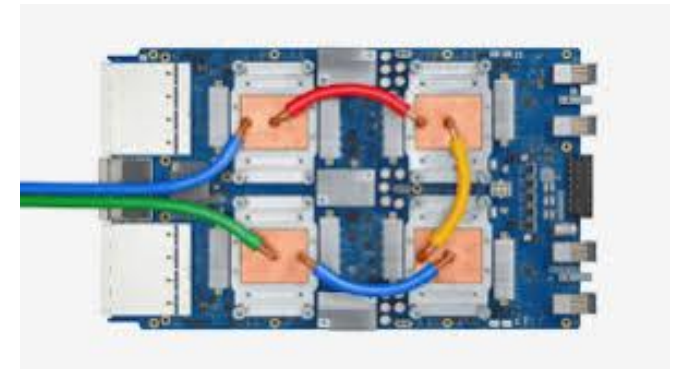

*The content of this lecture is adapted from the lectures of
Larry Zheng and Steve Engels*

CSCB58 Week 4: Summary



Week 4 Summary

We learned

- Sequential circuits – circuits with memory
- Latches
- Flip-flops


Latches

  - If multiple gates of these types (NAND or NOR with feedback) are combined, you can get more steady behaviour.




- These circuits are called **latches**.

S'R' Latch

 


S'R' latch

 

\bar{S}	\bar{R}	Q_T	\bar{Q}_T	Q_{T+1}	\bar{Q}_{T+1}
0	0	X	X	1	1
0	1	X	X	1	0
1	0	X	X	0	1
1	1	0	1	0	1
1	1	1	0	1	0


- S and R are called "set" and "reset" respectively.
- When $S' = 0$, $R' = 1$, Q is 1
- When $S' = 1$, $R' = 0$, Q is 0
- When $S'R' = 11$, same as previous state (01 or 10)
- How about going from 00 to 11
 - Depends on whether it changes from 00 to 01 to 11, or from 00 to 10 to 11 (race condition)
 - **unstable behaviour**

Clocked SR latch

 


- By adding another layer of NAND gates to the $\overline{S}\overline{R}$ latch, we end up with a **clocked SR latch** circuit.
- The clock is often connected to a pulse signal that alternates regularly between 0 and 1.

D latch

 

Edge-triggered flip-flop


- **Positive-edge triggered** flip-flops

 

- These are the most commonly-used flip-flop circuits (and our choice for the course).

 Question #1




- What are the output values from Q and \bar{Q} given the following inputs on S , R and C ?



Time





S	R	C	Q	\bar{Q}
0	0	1		
1	0	1		
1	0	0		
0	0	0		
0	1	0		
0	1	1		

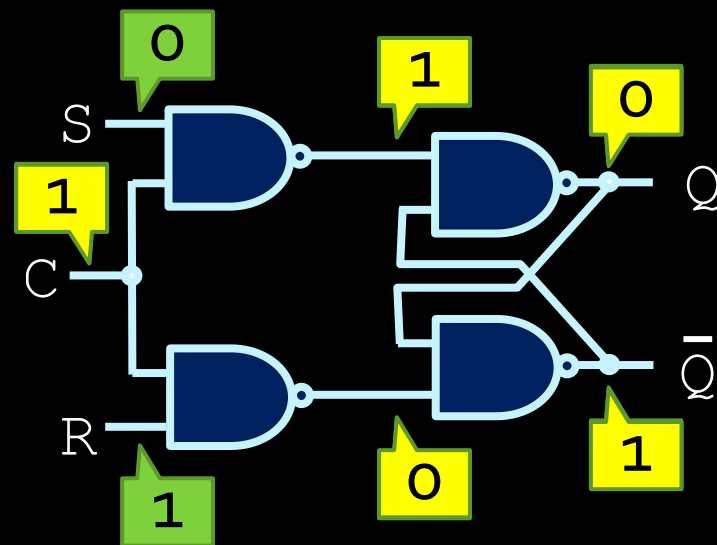 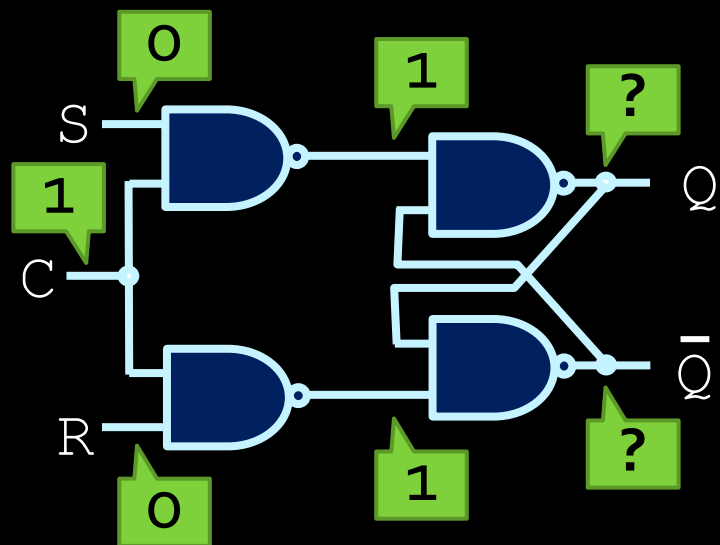

S	R	C	Q	\bar{Q}
0	0	1		
1	0	1		
1	0	0		
0	0	0		
0	1	0		
0	1	1		

 
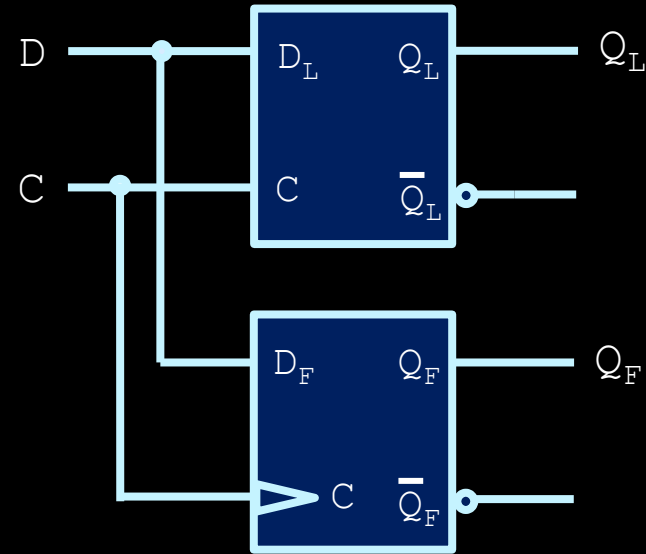
Question #2

- Given the circuit on the right and the input waveform below, what will the outputs be on Q_L and Q_F ?
 - What other info do you need?




Question #3

- Assuming the Q outputs of both flip-flops start off low, what will the value of X & Y be over the next few clock cycles?
 - also assume positive edge trigger.

 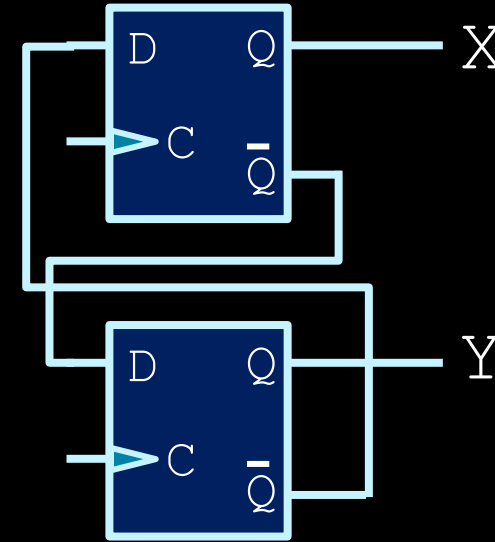


CSCB58: Computer Organization

 

Prof. Gennady Pekhimenko

University of Toronto

Fall 2020

 

*The content of this lecture is adapted from the lectures of
Larry Zheng and Steve Engels*